
PLL Presentation

Wiwitthawin Charoenngam 6310501933

$$K_{VCO} = 222.22 \text{ kHz/V}$$


$$R_{VCO} = 225 \text{ k}\Omega$$

$$R_{SET} = 43.61 \text{ k}\Omega$$


$$V_{ctrl(max)} = 2.1 \text{ V}$$

$$V_{ctrl(min)} = 1.2 \text{ V}$$

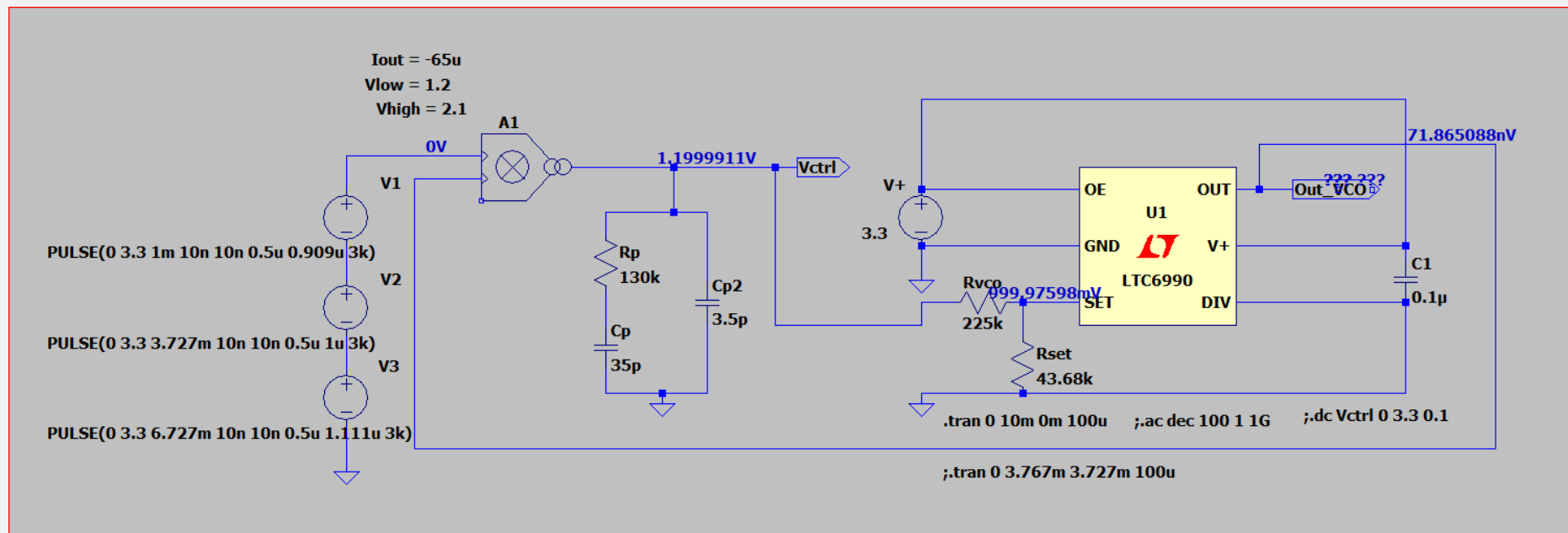
$$K_{PD} = 10.35 \frac{\mu\text{A}}{\text{rad/s}}$$




PLL Schematic

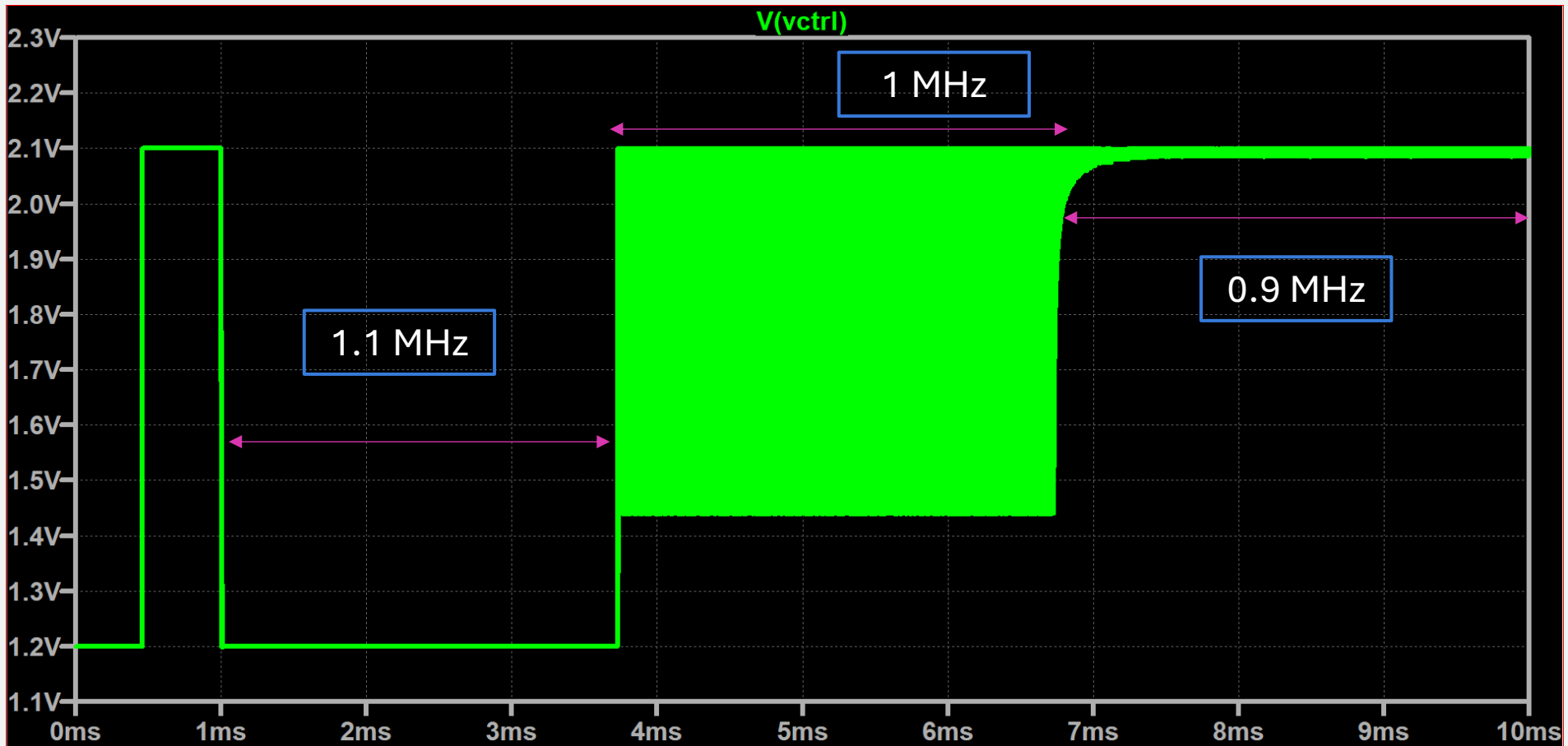

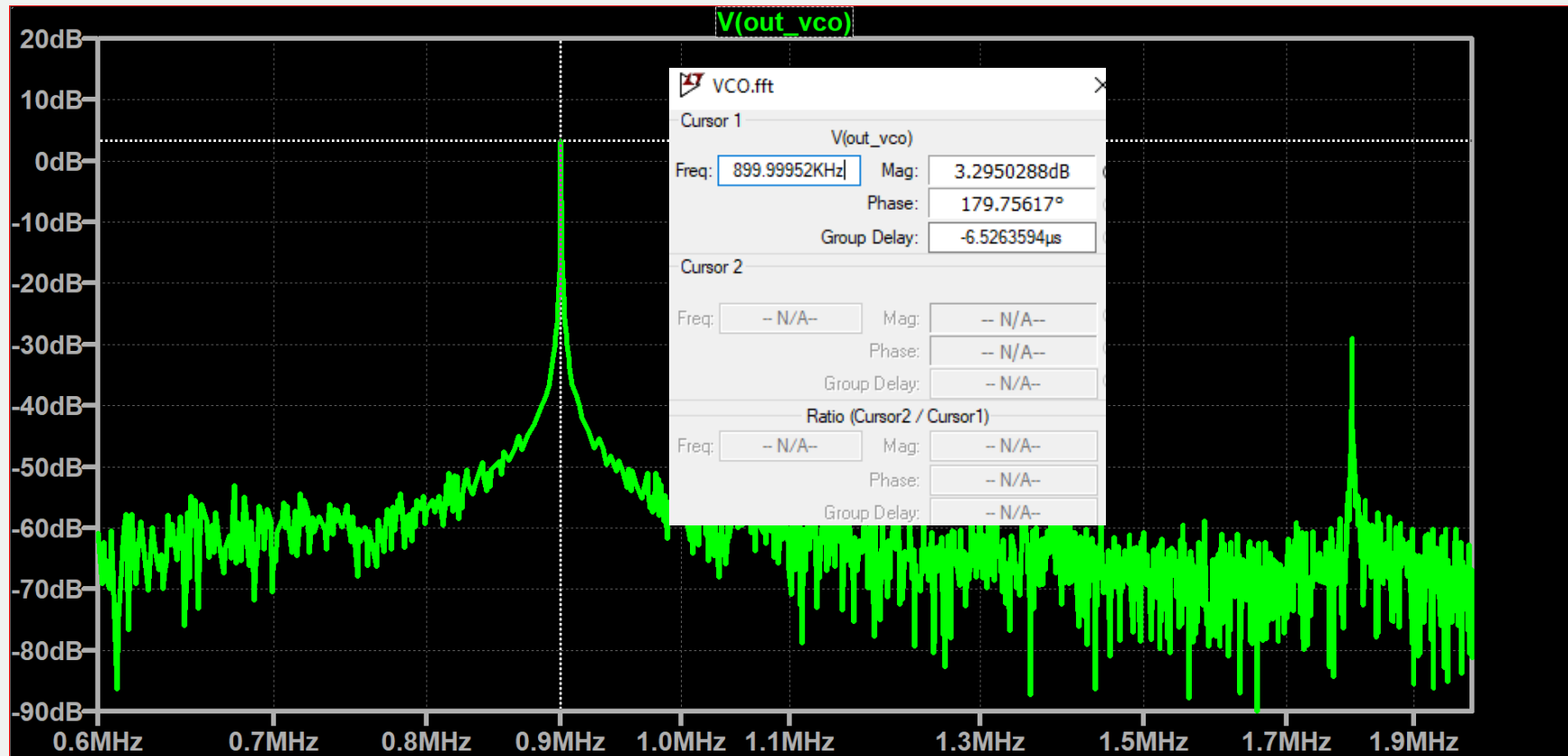
Control Voltage after using step frequency input



FFT of 0.9 MHz Output Voltage

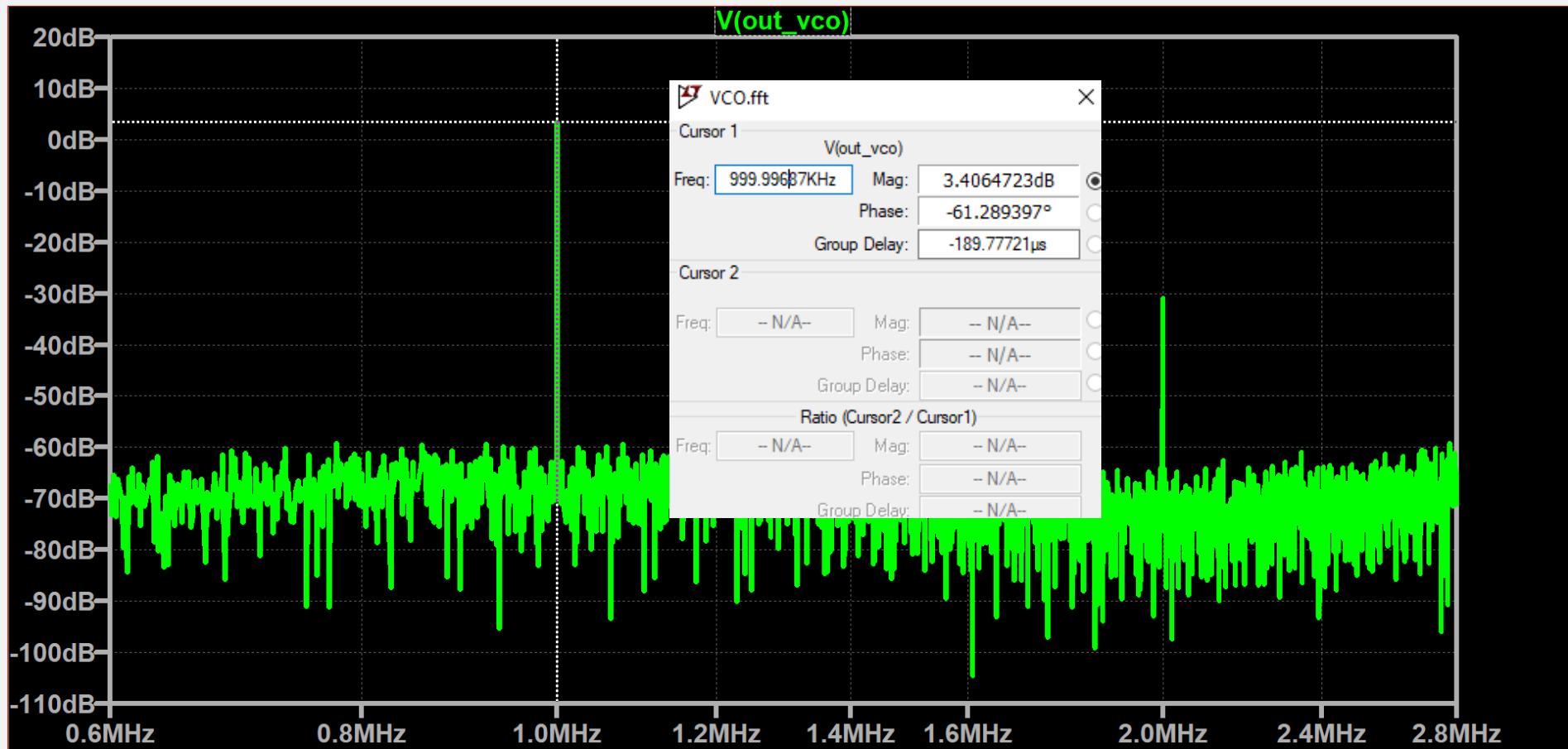


FFT of 1 MHz Output Voltage

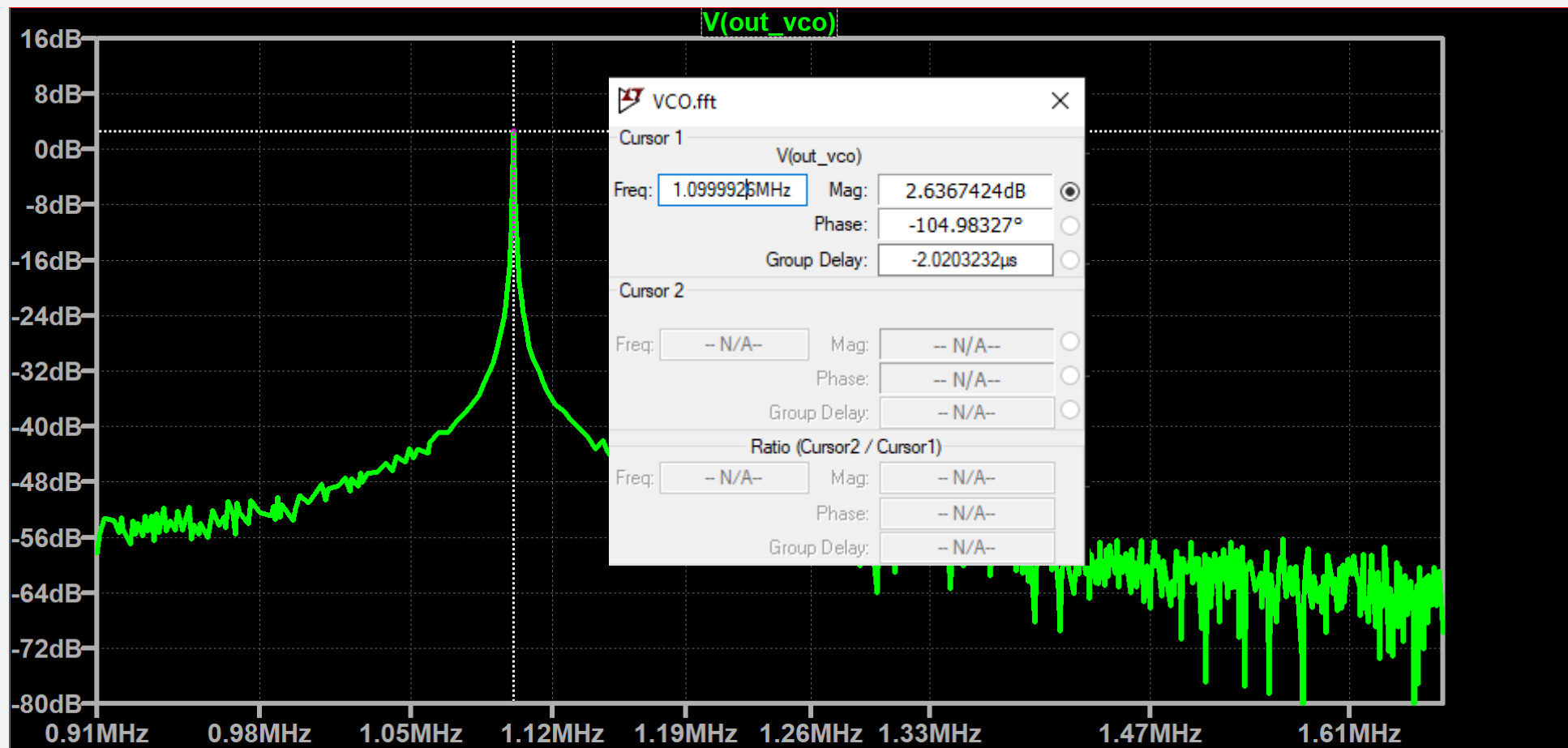

FFT of 1.1 MHz Output Voltage

MATLAB Modeling

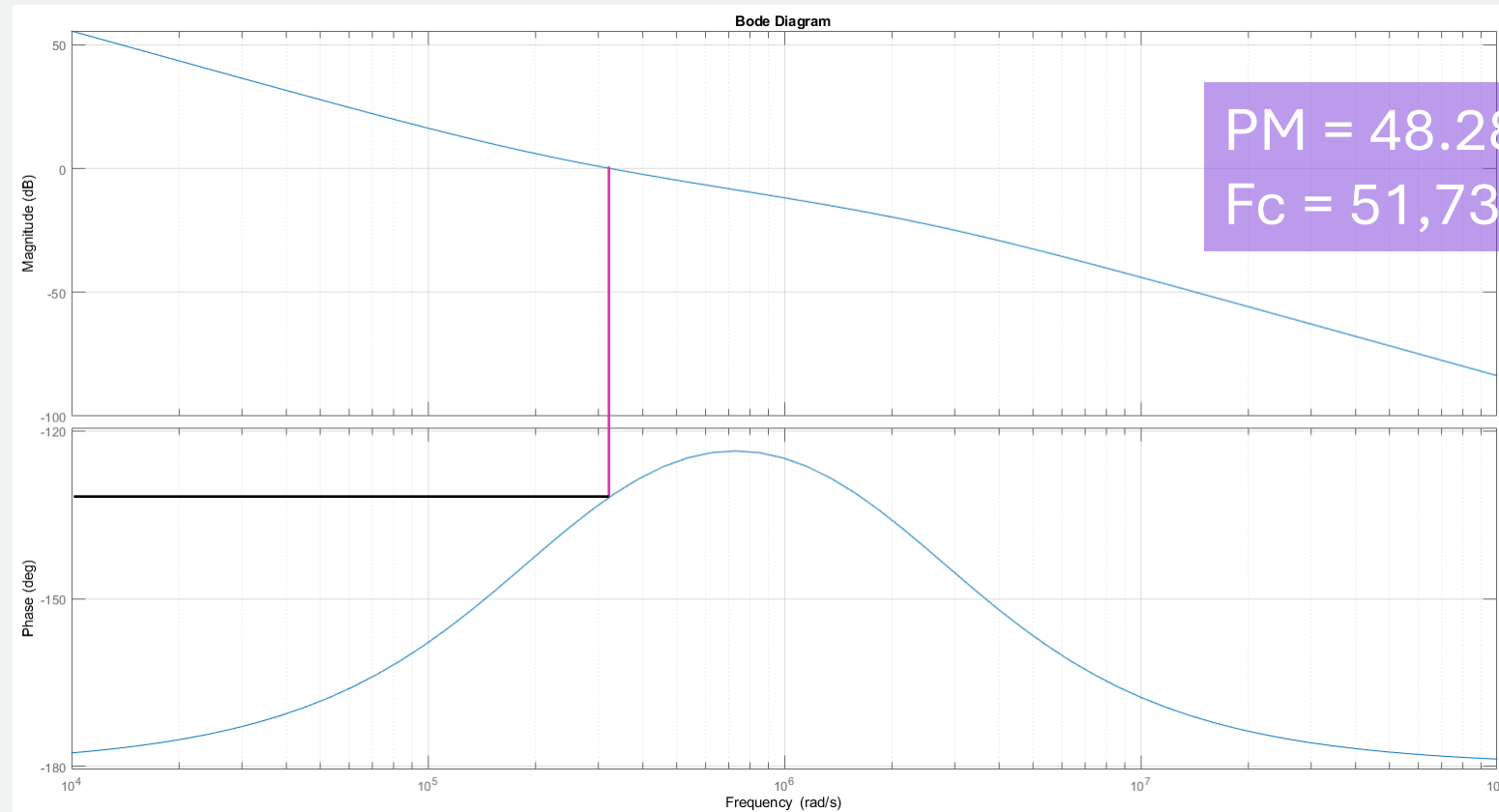

Bode plot of Theoretical modeling


MATLAB Modeling

Find Phase Margin and Crossover frequency by calculating the damping ratio from Overshoot and that of natural frequency from damping ratio and settling time for finding crossover frequency


$$\xi = \frac{-\ln(\frac{OS}{100})}{\sqrt{(\pi^2 + \ln^2(OS/100))}}, \quad TS = \frac{4}{\xi\omega_n},$$

$$PM = \tan^{-1}(2\xi\sqrt{(2\xi^2 + \sqrt{(4\xi^4 + 1))})})$$


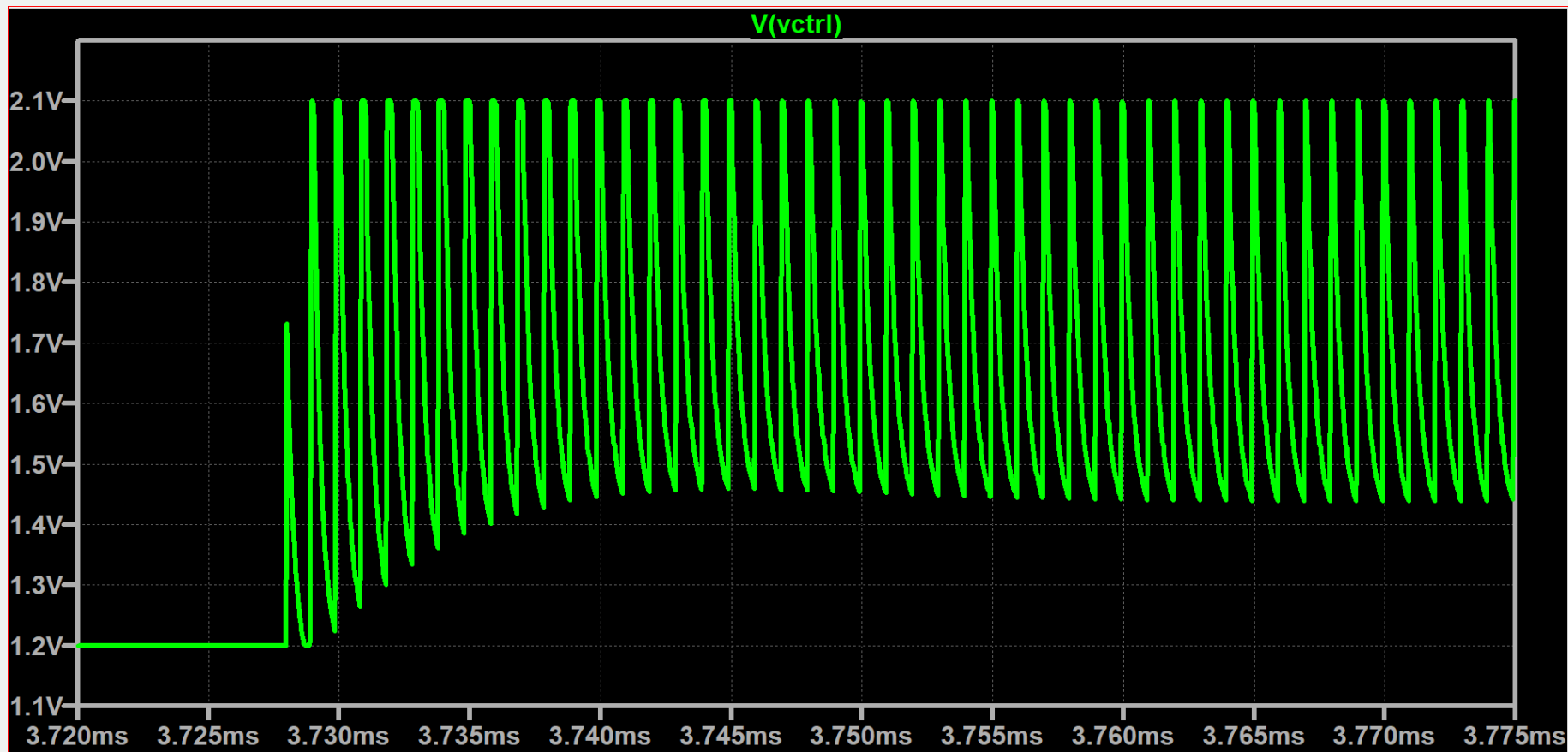
$$\omega_c = \omega_n * (\sqrt{(2\xi^2 + \sqrt{(4\xi^4 + 1))})})$$




Control Voltage of 1MHz pulse wave Input

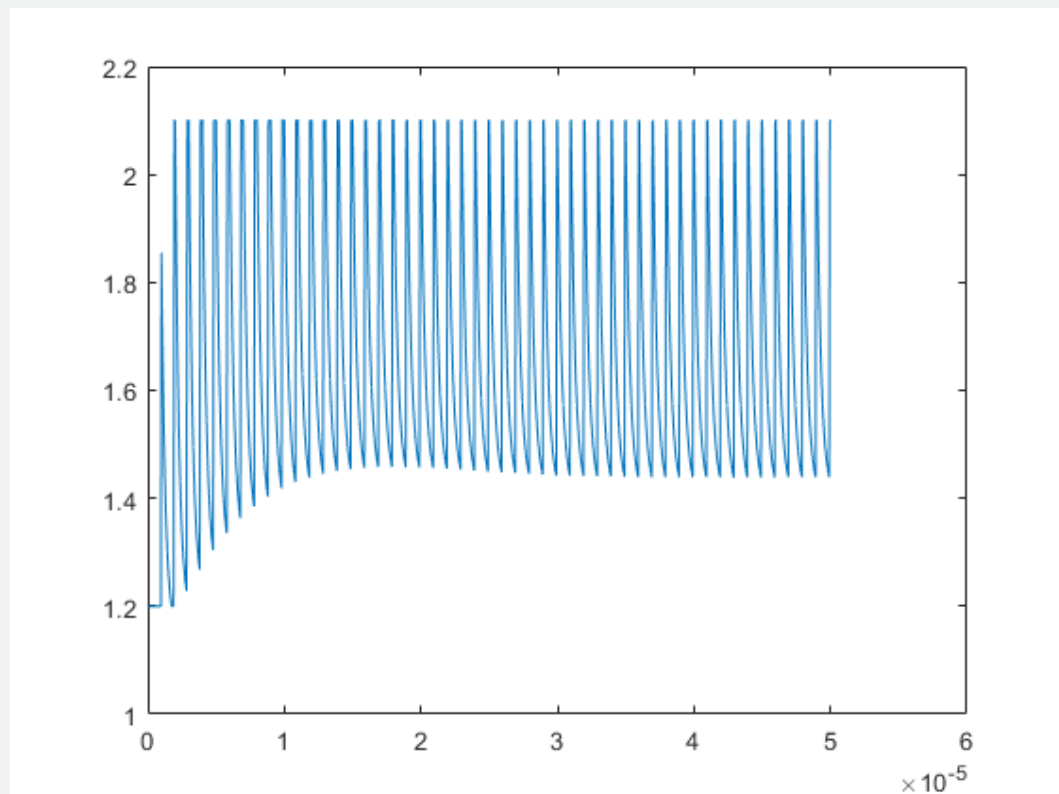

50 us time of 1 MHz step frequency

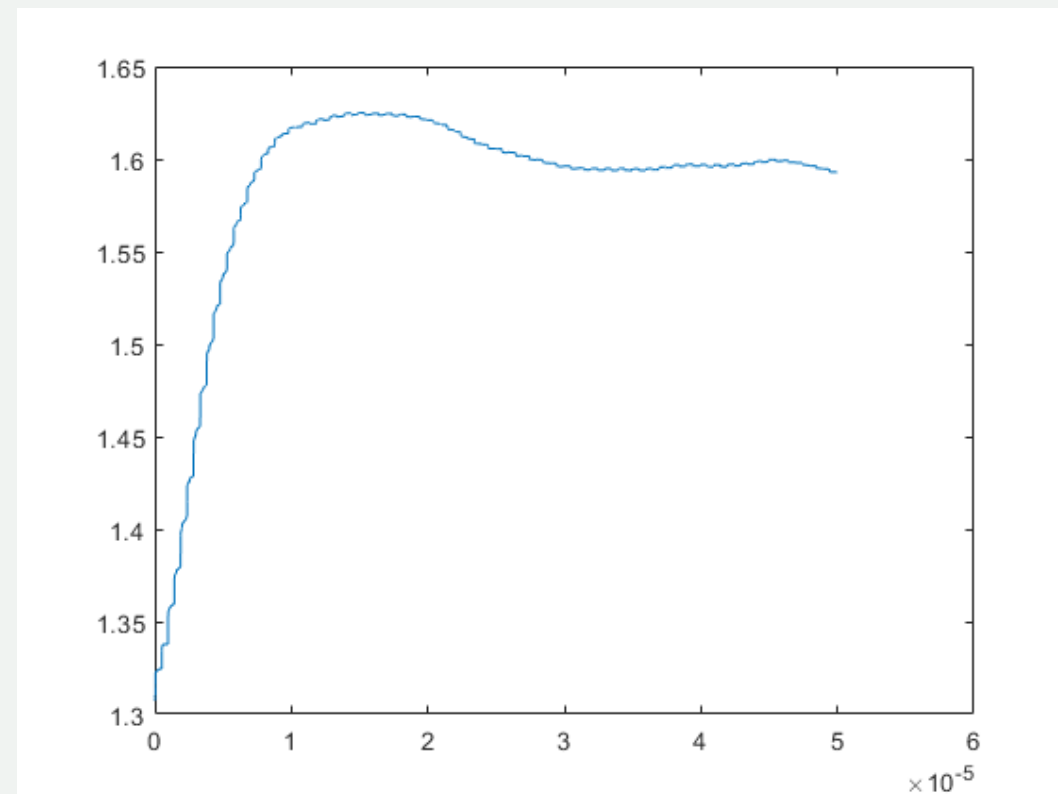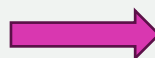

Smooth with gaussian 1400 taps

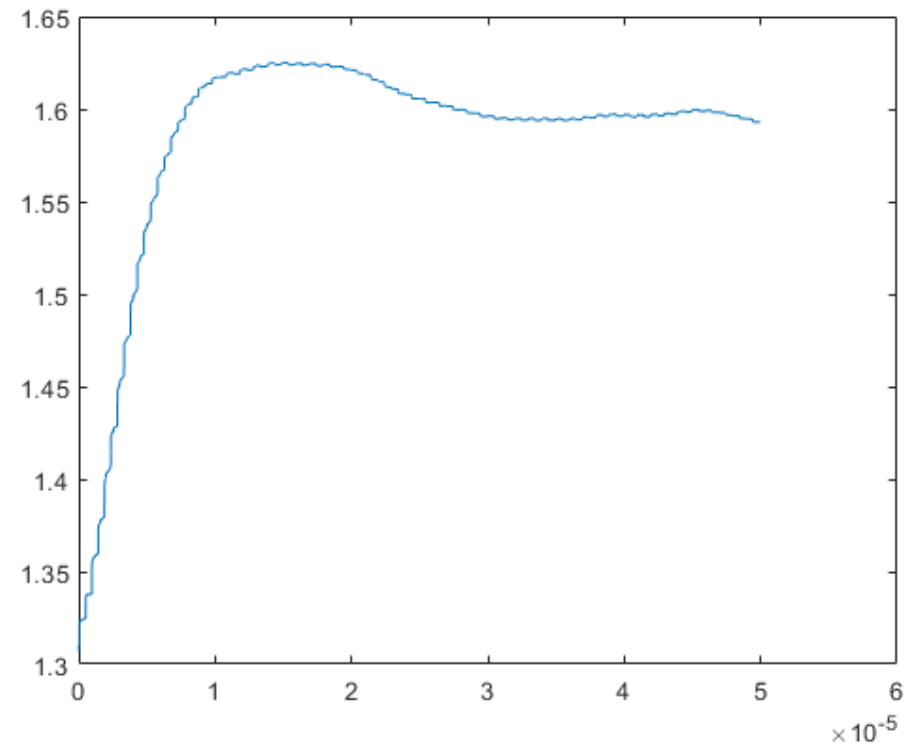

Smooth with gaussian 1400 taps

```
ans =
```

```
struct with fields:
```

```
    RiseTime: 2.8397e-06
  TransientTime: 4.6421e-05
    SettlingTime: 1.5369e-05
    SettlingMin: 1.4340
    SettlingMax: 1.6250
    Overshoot: 2.0042
    Undershoot: 0
        Peak: 1.6250
    PeakTime: 1.5132e-05
```

```
Fcross =
```

```
5.3982e-04
```

```
PM =
```

```
69.8866
```

Summary

With Design, 2 % Overshoot and 15.37 us Settling time is achieved, resulting in 69.89 Phase margin and 53.98 kHz Crossover frequency. PLL can be locked within 0.9 – 1.1 MHz with 53.98 kHz crossover frequency and 69.89-degree phase margin

**Thank you for
listening**
